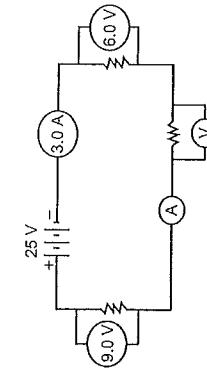


Series Circuits**Goal** • Review your understanding of series circuits.**What to Do**


Circle the best term in the parentheses to correctly complete each statement.

- A series circuit has (*more than one, only one*) path for current to travel.
- In a series circuit, the current at one location in the circuit is (*equal to, different from*) the current at another location in the circuit.
- If two different resistors are connected in series, the voltage across one resistor will be (*equal to, different from*) the voltage across the second resistor.
- By adding a resistor in series with an original resistor, the total resistance of the circuit (*increases, decreases*).
- The sum of the voltages across each of the resistors in a series circuit is (*equal to, different from*) the voltage supplied by the battery.

Find the unknown voltage at V, and current at A, in each of the following circuits.



6. Voltage = _____
Current = _____

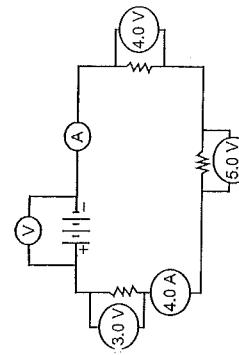


7. Voltage = _____
Current = _____

Goal • Review your understanding of parallel circuits.**What to Do**


Circle the best term in the parentheses to correctly complete each statement.

- A parallel circuit has (*only one, more than one*) path for current to travel.
- Two different resistors are connected in parallel. The current through one of the resistors will be (*equal to, different from*) the current through the other resistor.
- If two different resistors are connected in parallel, the voltage across one resistor will be (*equal to, different from*) the voltage across the second resistor.
- By adding a resistor in parallel with an original resistor, the total resistance of the circuit (*increases, decreases*).
- The total current entering the junction of a parallel circuit must be (*equal to, different from*) the sum of the currents through each branch of the parallel circuit.

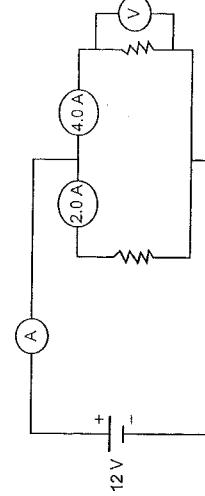Find the unknown voltage at V, and current at A, in each of the following circuits.



6. Voltage = _____
Current = _____

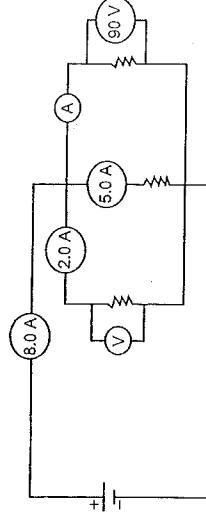

7. Voltage = _____
Current = _____

DATE: NAME:

CLASS:


BLW 3-17

CHAPTER 8 Calculate the Current

Goal • Practise calculating current.

What to Do

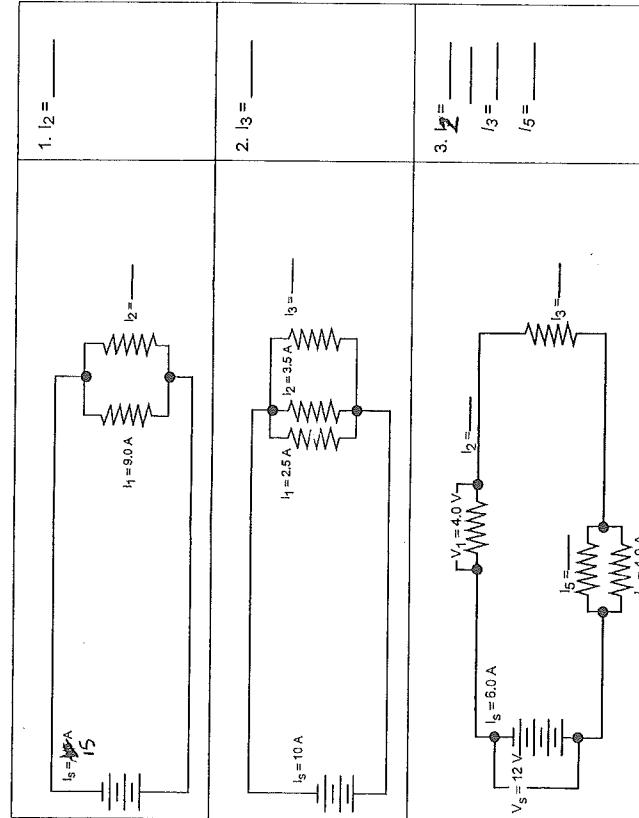Calculate the current in each of the following circuit diagrams. The current at the source is represented by I_s



DATE: NAME:

CLASS:

BLW 3-18


CHAPTER 8 Calculate the Potential Difference


Goal • Practise potential difference calculations.

What to Do

Calculate the missing potential difference in each of the following circuit diagrams. The voltage at the source is represented by V_s [V_s]

Diagrams

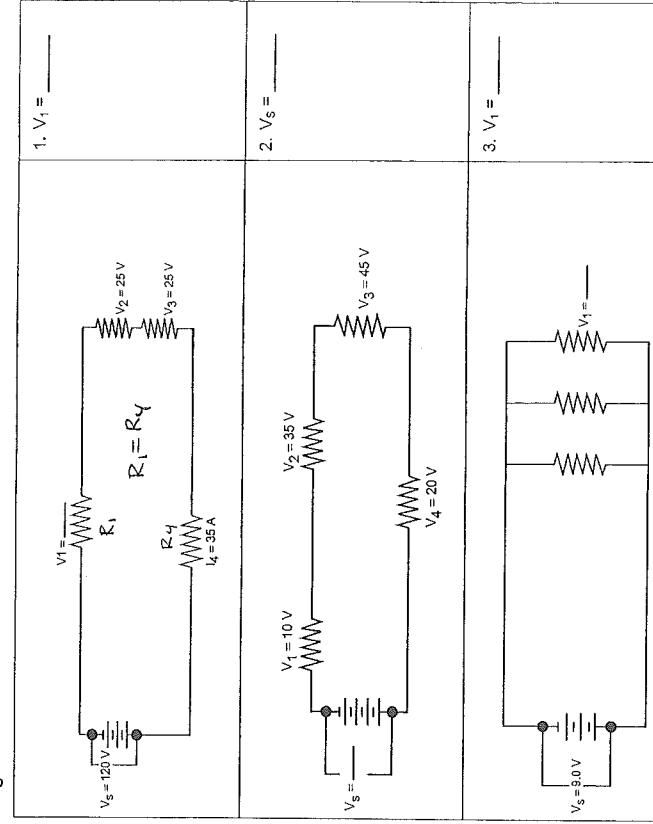


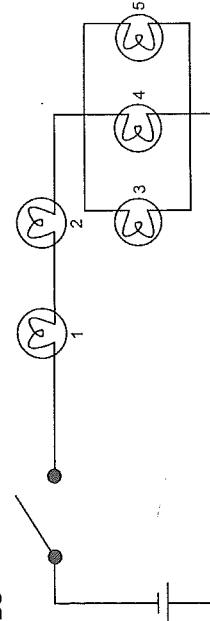**Goal** • Practise interpreting circuit diagrams.**What to Do**

1. Describe what will happen in the circuit shown above if...

- (a) the switch is closed _____
- (b) the switch is closed and the first bulb is removed _____
- (c) the switch is closed and the fifth bulb is removed _____

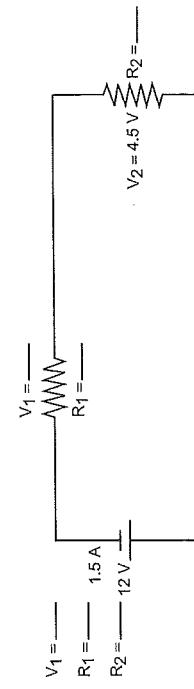2. Calculate the missing quantities for the circuit below.



3. Calculate the missing quantities for the circuit below.

