

CHAPTER 9 Parallel Circuits **BLM 3-29**

Goal • Review your understanding of parallel circuits.


What to Do

Circle the best term in the parentheses to correctly complete each statement.


1. A parallel circuit has (*only one*, more than one) path for current to travel.
2. Two different resistors are connected in parallel. The current through one of the resistors will be (*equal to*, different from) the current through the other resistor.
3. If two different resistors are connected in parallel, the voltage across one resistor will be (equal to, *different from*) the voltage across the second resistor.
4. By adding a resistor in parallel with an original resistor, the total resistance of the circuit (*increases*, decreases) *Think of a traffic jam & a new lane opens*
5. The total current entering the junction of a parallel circuit must be (equal to, *different from*) *up* the sum of the currents through each branch of the parallel circuit.

Find the unknown voltage at V, and current at A, in each of the following circuits.

6. Voltage = 12 V
 Current = 6 A

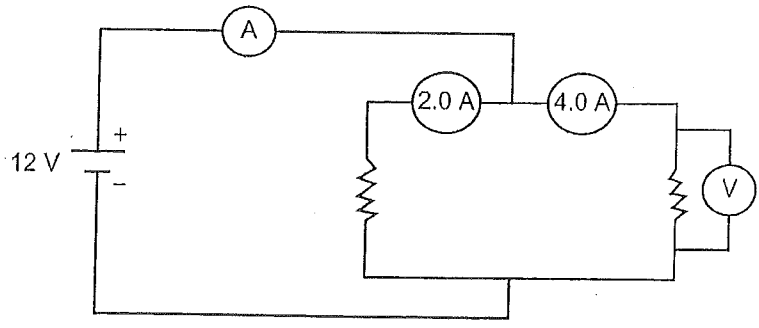

7. Voltage = 90 V
 Current = 1 A

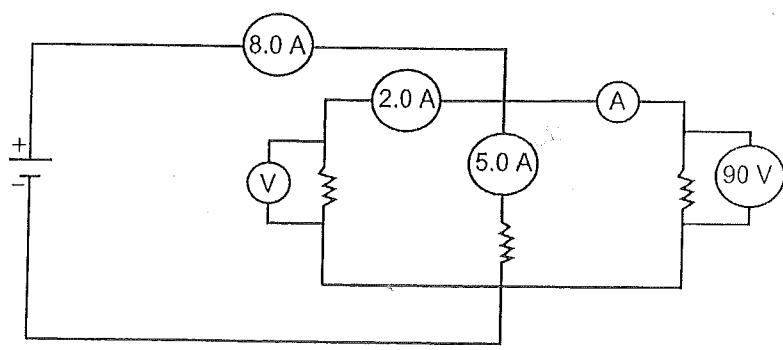

Goal • Review your understanding of series circuits.

What to Do

Circle the best term in the parentheses to correctly complete each statement.

1. A series circuit has (*more than one*, only one) path for current to travel.
2. In a series circuit, the current at one location in the circuit is (equal to, *different from*) the current at another location in the circuit.
3. If two different resistors are connected in series, the voltage across one resistor will be (*equal to*, different from) the voltage across the second resistor.
4. By adding a resistor in series with an original resistor, the total resistance of the circuit (increases, *decreases*).
5. The sum of the voltages across each of the resistors in a series circuit is (equal to, *different from*) the voltage supplied by the battery.


Find the unknown voltage at V, and current at A, in each of the following circuits.

6. Voltage =

10V

Current =

3A

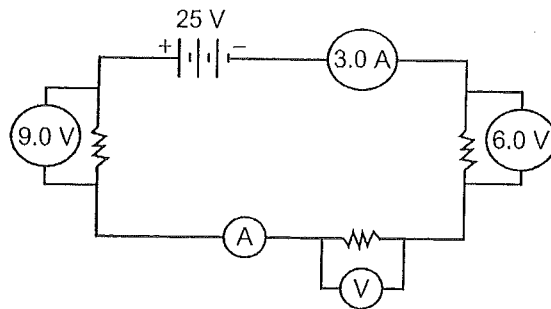


$$3 + 6 = 9V$$

7. Voltage =

12V

Current =

4A

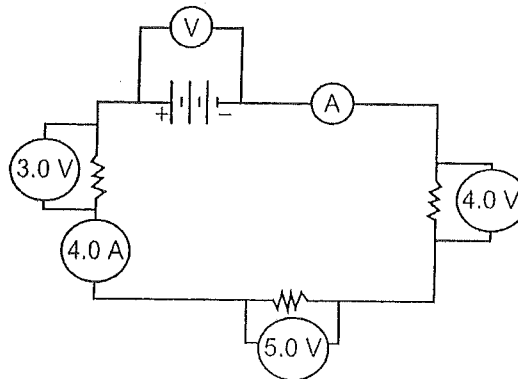

Goal • Practise calculating current.

What to Do

Calculate the current in each of the following circuit diagrams. The current at the source is represented by I_s

$I_{\text{series}} \rightarrow I_T = I_1 = I_2$
 $I_{\text{parallel}} \rightarrow I_T = I_1 + I_2$

	<p>1. $I_2 = \underline{6}$</p>
	<p>2. $I_3 = \underline{4}$</p>
	<p>3. $I_3 = \underline{6}$ $I_5 = \underline{2}$ $I_5 = \underline{4}$ $I_5 = \underline{2}$</p>

Goal • Practise potential difference calculations.

What to Do

$$V_{\text{series}} \quad V_T = V_1 + V_2$$

$$V_{\text{parallel}} \quad V_T = V_1 = V_2$$


Calculate the missing potential difference in each of the following circuit diagrams. The voltage at the source is represented by V_s [V_s]

Diagrams

<p>$V_s = 120\text{V}$</p> <p>$V_1 = 35\text{V}$</p> <p>$R_1 = R_4$</p> <p>$V_1 = V_4$</p> <p>$V_2 = 25\text{V}$</p> <p>$V_3 = 25\text{V}$</p> <p>$V_4 = 35\text{V}$</p>	<p>1. $V_1 = 35\text{V}$</p> <p>$V_1 = 120 - 85 = 35$</p> <p>$V_2 + V_3 + V_4 = 25 + 25 + 35 = 85$</p>
<p>$V_s =$</p> <p>$V_1 = 10\text{V}$</p> <p>$V_2 = 35\text{V}$</p> <p>$V_3 = 45\text{V}$</p> <p>$V_4 = 20\text{V}$</p>	<p>2. $V_s = 110\text{V}$</p> <p>$V_s = V_1 + V_2 + V_3 + V_4$</p> <p>$= 10 + 35 + 45 + 20$</p> <p>$= 110\text{V}$</p>
<p>$V_s = 9.0\text{V}$</p> <p>$V_1 = 9\text{V}$</p>	<p>3. $V_1 = 9\text{V}$</p>

Goal • Practise interpreting circuit diagrams.


What to Do

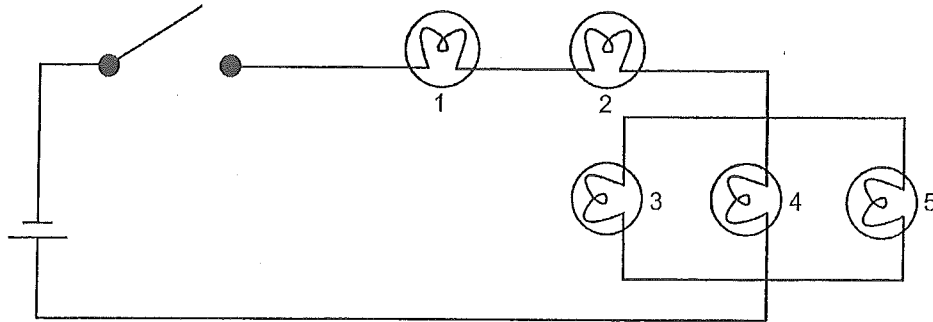


1. Describe what will happen in the circuit shown above if...

- (a) the switch is closed the bulbs will light
- (b) the switch is closed and the first bulb is removed bulbs will not light
- (c) the switch is closed and the fifth bulb is removed all other bulbs will stay lit

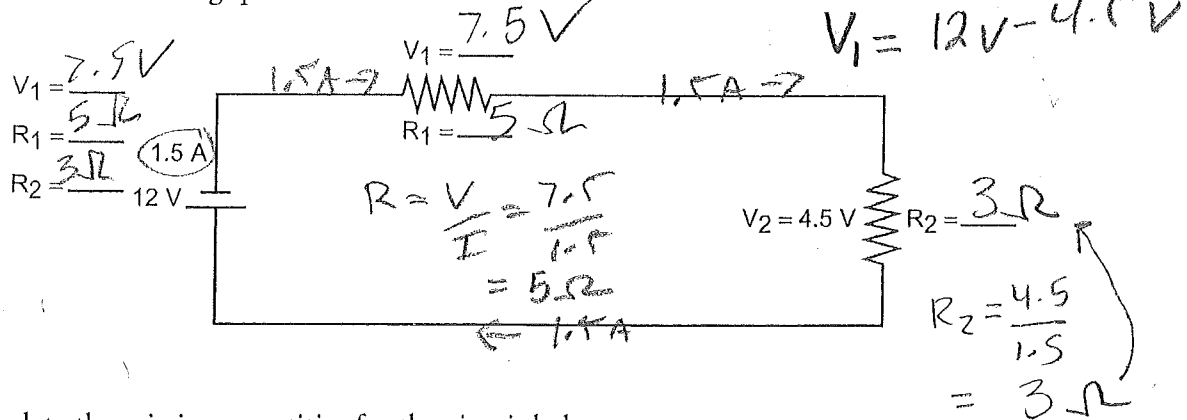2. Calculate the missing quantities for the circuit below.



3. Calculate the missing quantities for the circuit below.

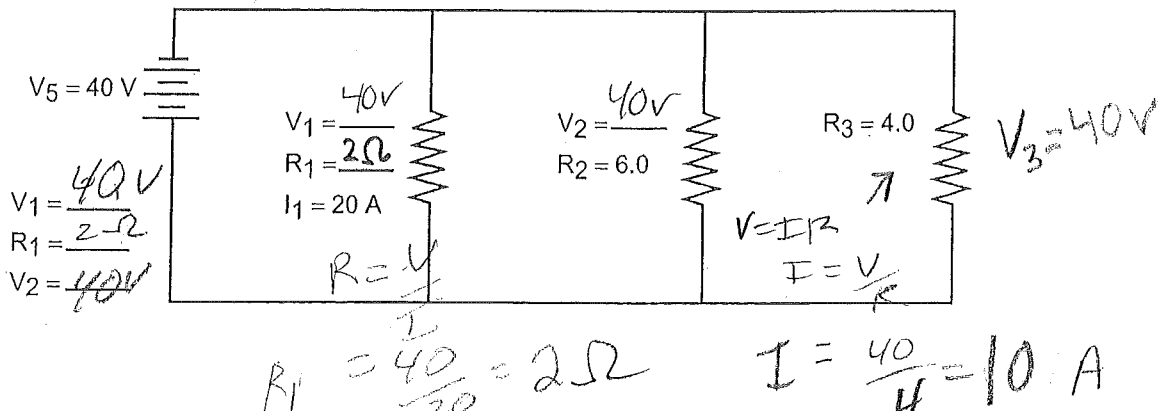

CHAPTER 9

Calculate Voltage and Current


BLM 3-33

Goal • Practise calculating voltage and current in a circuit.

What to Do

Calculate the missing values in the circuits below. Be sure to show your calculations.

1.

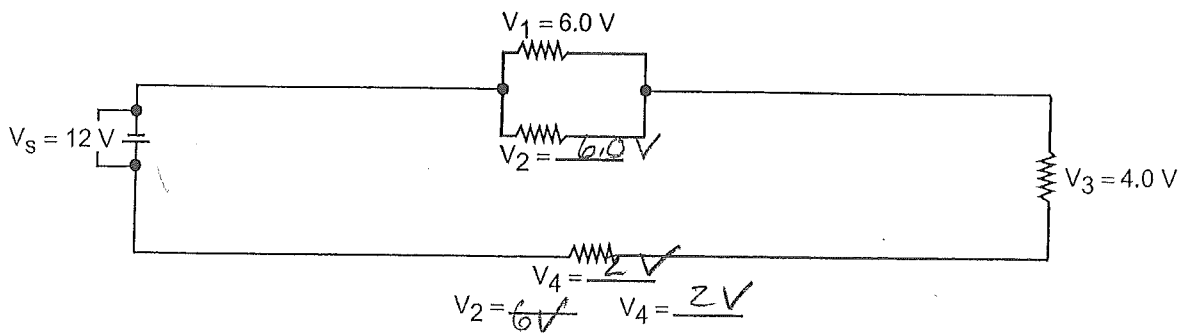

2.

